



## 1 Q factor of a Resonance Circuit

We define a “quality factor”,  $Q \equiv \frac{\omega_0}{2\beta}$ , and use it as a measure of cycles in a free (undriven), damped oscillator before the oscillation decays to some smaller amplitude. The larger the number of cycles, the larger the  $Q$ . Now let’s see what this quantity translates to in a driven, damped oscillator. Use the example of charge amplitude  $|q|$  for a series LRC circuit.

- Show that at both frequencies  $\omega = \omega_0 + \beta$  and  $\omega = \omega_0 - \beta$ , the magnitude of the charge response  $|q|$  is  $\frac{|q|_{max}}{\sqrt{2}}$ .  
(Hint – this is a 3-line calculation. You don’t need the definition of  $|q|$  in terms of  $L, R, C$ ).
- At these frequencies, how large is the energy in the capacitor compared to the maximal energy at  $\omega \approx \omega_0$ ?
- Given the above, operationally, how would you measure the  $Q$  of a resonant circuit? What is  $Q$  for your circuit?

The graphs below may help with a visual feel for the quantities discussed above:

## 2 Steady State Solutions for the LRC Circuit

- Write the equation of motion governing the charge on the capacitor in a series LRC circuit driven by an external sinusoidal voltage. Identify all parameters in your equation.
- Find a steady-state solution (or particular solution) for the *current* in the circuit. After what time is the steady state the only relevant part of the solution, *i.e.*, after what time has the transient solution decayed for the circuit you are working with?
- Find the steady state solution for  $\frac{dI}{dt}$  in this circuit.